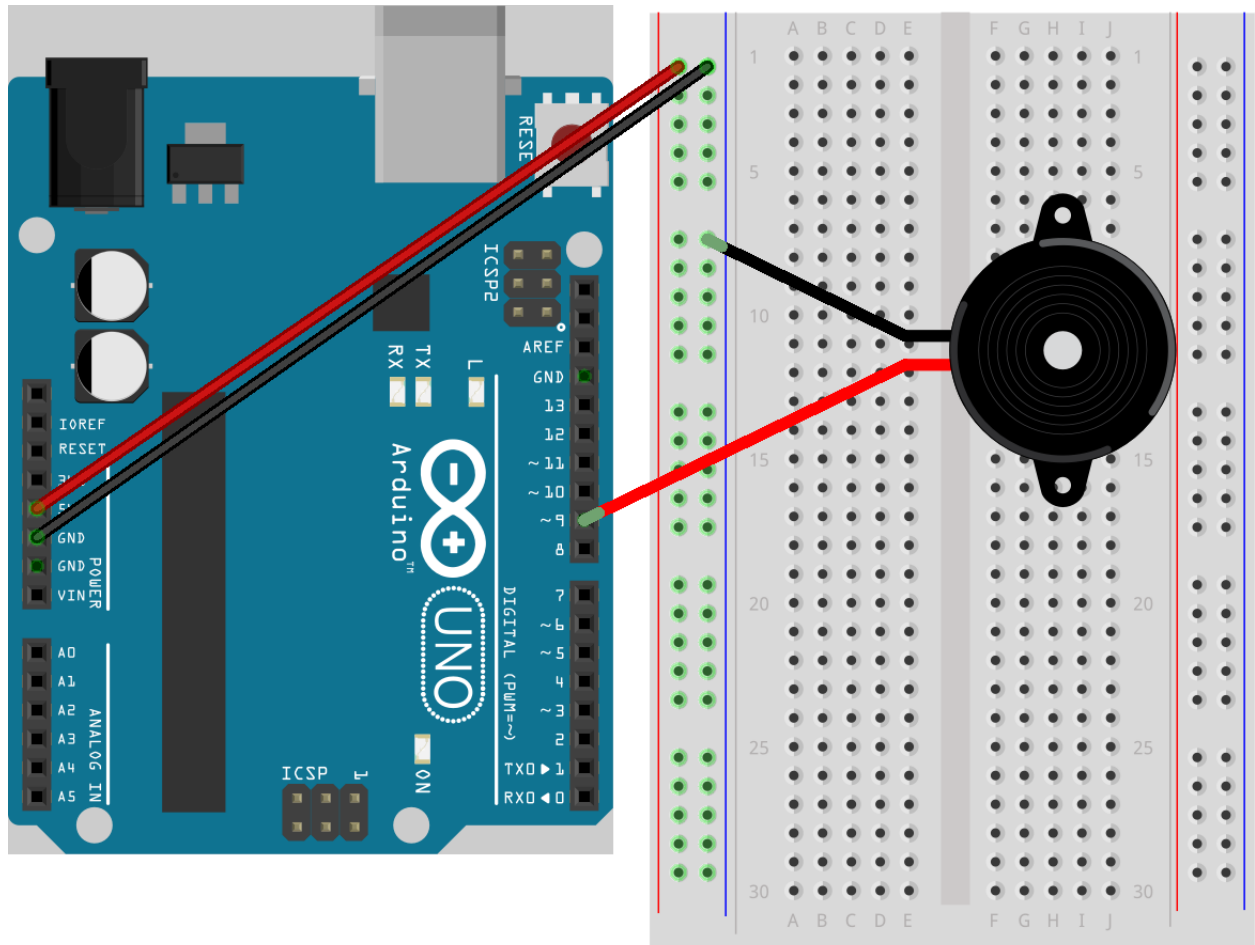


Piezo Circuit



fritzing

Circuit Steps:

1. Connect the **Arduino 5V** to the **+ rail** on the breadboard.
2. Connect the **Arduino GND** to the **- rail** on the breadboard.
3. Connect **one leg of the piezo** to the **- rail** on the breadboard.
4. Connect **one leg of the piezo** to a **digital pin** on the Arduino. In this example, the connection is to digital pin 9.